






Sample: Electric Circuits - Circuits with Capacitors

World of the electron: coursework 1

Show all workings, including diagrams where appropriate.

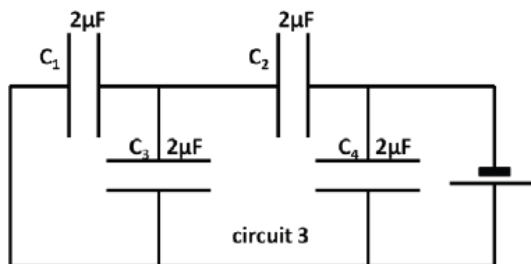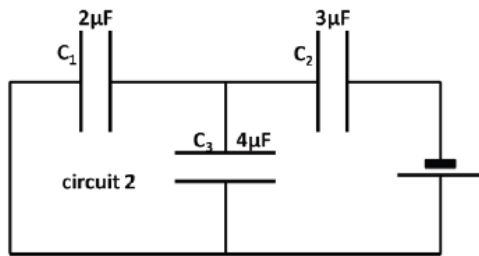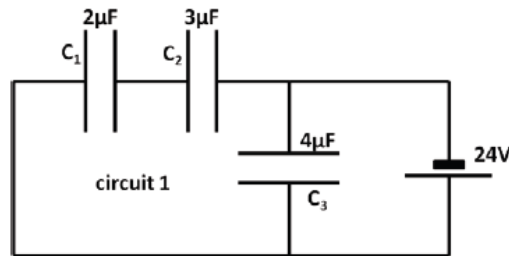- 1) For each of the circuits shown below, calculate the total equivalent capacitance of the circuit. [10 marks]
- 2) For circuit 1, calculate the total amount of energy stored by this equivalent capacitance. [2 marks]
- 3) For circuit 1, calculate the charge on each capacitor and the potential difference across each capacitor. [8 marks]





1.

$$\begin{aligned} C_1 &= 2 \mu F \\ C_2 &= 3 \mu F \\ C_3 &= 4 \mu F \end{aligned}$$

I circuit:

$$\begin{aligned} \frac{1}{C_{12}} &= \frac{1}{C_1} + \frac{1}{C_2} = \frac{C_2 + C_1}{C_1 C_2} \\ C_{12} &= \frac{C_1 C_2}{C_1 + C_2} \end{aligned}$$

Now for the whole circuit:

$$\begin{aligned} C &= C_3 + C_{12} = C_3 + \frac{C_1 C_2}{C_1 + C_2} = \frac{C_3(C_1 + C_2) + C_1 C_2}{C_1 + C_2} = \frac{C_1 C_3 + C_2 C_3 + C_1 C_2}{C_1 + C_2} \\ &= \frac{2 \mu F \times 4 \mu F + 3 \mu F \times 4 \mu F + 2 \mu F \times 3 \mu F}{2 \mu F + 3 \mu F} = \frac{8 + 12 + 6}{5} \mu F = \frac{26}{5} \mu F \\ &= 5.2 \mu F \end{aligned}$$

II circuit:

$$\begin{aligned} C_{13} &= C_1 + C_3 \\ \frac{1}{C} &= \frac{1}{C_{13}} + \frac{1}{C_2} = \frac{1}{C_1 + C_3} + \frac{1}{C_2} = \frac{C_2 + C_1 + C_3}{C_2(C_1 + C_3)} \\ C &= \frac{C_2(C_1 + C_3)}{C_1 + C_2 + C_3} = \frac{3(2 + 4)}{2 + 3 + 4} \mu F = \frac{18}{9} \mu F = 2 \mu F \end{aligned}$$

III circuit:

$$\begin{aligned} C_1 &= 2 \mu F \\ C_2 &= 3 \mu F \\ C_3 &= 4 \mu F \\ C_4 &= 2 \mu F \\ C_{13} &= C_1 + C_3 \\ \frac{1}{C_{123}} &= \frac{1}{C_{13}} + \frac{1}{C_2} = \frac{1}{C_1 + C_3} + \frac{1}{C_2} = \frac{C_2 + C_1 + C_3}{C_2(C_1 + C_3)} \\ C_{123} &= \frac{C_2(C_1 + C_3)}{C_1 + C_2 + C_3} \\ C_{1234} &= C_{123} + C_4 = \frac{C_2(C_1 + C_3)}{C_1 + C_2 + C_3} + C_4 = \frac{C_1 C_2 + C_2 C_3 + C_1 C_4 + C_2 C_4 + C_3 C_4}{C_1 + C_2 + C_3} \\ &= \frac{2 \times 3 + 3 \times 4 + 2 \times 2 + 2 \times 2 + 4 \times 2}{2 + 3 + 4} = \frac{6 + 12 + 4 + 4 + 8}{9} \mu F \\ &= \frac{34}{9} \mu F = 3.77 \mu F \end{aligned}$$

2.

$$C_{1circuit} = 5.2 \mu F$$

Total amount of energy stored:

$$W = \frac{CU^2}{2} = \frac{5.2 \mu F \times (24 V)^2}{2} = \frac{5.2 \mu F \times 576 V^2}{2} = 1497.6 J$$



3.

Let's use charge conservation law:

$$q_1 + q_2 + q_3 = 0$$
$$E = U_3 = U_1 + U_2 = 24 V$$

By definition:

$$q_3 = C_3 U_3 = 4 \mu F \times 24 V = 96 \times 10^{-6} C$$
$$q_2 = C_2 U_2$$
$$q_1 = C_1 U_1$$

Let's also use formula

$$U_2 = E - U_1$$

From first we get:

$$q_1 = -q_2 - q_3 = -C_2 U_2 - q_3 = -C_2 (E - U_1) - q_3 = C_1 U_1$$

From where we get U_1 :

$$C_1 U_1 = -C_2 E + C_2 U_1 - q_3$$
$$U_1 (C_2 - C_1) = C_2 E + q_3$$
$$U_1 = \frac{C_2 E + q_3}{C_2 - C_1} = \frac{3 \mu F \times 24 V + 96 C}{(3 - 2) \mu F} = 168 V$$
$$U_2 = E - U_1 = 24 V - 168 V = -144 V$$

Minus sign shows us that charge would be negative.

$$q_1 = C_1 U_1 = 2 \mu F \times 168 V = 336 \times 10^{-6} C$$
$$q_2 = C_2 U_2 = 3 \mu F \times -144 V = -432 \times 10^{-6} C$$