

Question #75004 - Math - Calculus

A transmission line with characteristic impedance 250Ω is connected to a pure resistive load of 1000Ω through a $\lambda/4$ line segment. Calculate the characteristic impedance of this segment to achieve perfect matching between the load and the transmission line.

Solution: input impedance of transmission line:

$$Z_{in}(l) = Z_0 \frac{Z_L + Z_0 \cdot \tanh(\gamma l)}{Z_0 + Z_L \cdot \tanh(\gamma l)}$$

$Z_0 = 250$ – characteristic impedance

$Z_L = 1000$ – load resistance

γ – propagation constant

l – length of transmission line

input impedance of lossless transmission line:

$$Z_{in}(l) = Z_0 \frac{Z_L + j \cdot Z_0 \cdot \tan(\beta l)}{Z_0 + j \cdot Z_L \cdot \tan(\beta l)}$$

$$\beta = \frac{2\pi}{\lambda} \text{ – wavenumber}$$

for $\lambda/4$ line segment:

$$Z = \frac{Z_0^2}{Z_L} = \frac{250^2}{1000} = 62.5 \Omega$$

Answer: $Z = 62.5 \Omega$

Answer provided by <https://www.AssignmentExpert.com>