

## Answer on Question #78800 – Math – Differential Equations

Charging characteristics for a series capacitive circuit is

$$V_C = V \left( 1 - e^{-\frac{t}{T}} \right),$$

where  $T = CR$ , time is constant;

Capacitor,  $C = 100 \text{ nF}$ ;

Resistor,  $R = 47 \text{ k}\Omega$ ;

Supply voltage,  $V = 5 \text{ Volts}$ .

### Question

1. Determine the value of  $t$  when  $V_C = 4.15 \text{ Volts}$ .

### Solution

$$V_C = V \left( 1 - e^{-\frac{t}{T}} \right)$$

Solve for  $t$

$$1 - e^{-\frac{t}{T}} = \frac{V_C}{V}$$

$$e^{-\frac{t}{T}} = 1 - \frac{V_C}{V}$$

$$-\frac{t}{T} = \ln \left( 1 - \frac{V_C}{V} \right)$$

$$t = -T \ln \left( 1 - \frac{V_C}{V} \right)$$

$$t = -RC \ln \left( 1 - \frac{V_C}{V} \right)$$

Substitute

$$t = -(47 \times 10^3 \Omega)(100 \times 10^{-9} \text{ F}) \ln \left( 1 - \frac{4.15 \text{ Volts}}{5 \text{ Volts}} \right)$$

$$t = 0.00832820 \text{ s} \approx 8.328 \times 10^{-3} \text{ s} = 8.328 \text{ ms}$$

**Answer:**  $t = 8.328 \text{ ms}$

### Question

2. Differentiate the charging equation and find the rate of change of voltage at  $6 \text{ ms}$ .

### Solution

$$V_C = V \left( 1 - e^{-\frac{t}{T}} \right)$$

Differentiate both sides with respect to  $t$

$$\frac{d}{dt}(V_C) = \frac{d}{dt} \left( V \left( 1 - e^{-\frac{t}{T}} \right) \right)$$

$$\text{rate of change of voltage} = \frac{dV_C}{dt} = V \left( \frac{1}{T} \right) e^{-\frac{t}{T}} = \frac{V}{RC} e^{-\frac{t}{RC}}$$

Capacitor,  $C = 100 \text{ nF}$

Resistor,  $R = 47 \text{ k}\Omega$

Supply voltage,  $V = 5 \text{ Volts}$

$t = 6 \text{ ms}$

$$\begin{aligned} \text{rate of change of voltage} &= \frac{dV_C}{dt} = \\ &= \frac{5 \text{ Volts}}{(47 \times 10^3 \Omega)(100 \times 10^{-9} \text{ F})} e^{-\frac{6 \times 10^{-3} \text{ s}}{(47 \times 10^3 \Omega)(100 \times 10^{-9} \text{ F})}} \approx 296.793 \text{ Volts/s} \end{aligned}$$

$$\text{Answer: rate of change of voltage} = \frac{dV_C}{dt} = V \left( \frac{1}{T} \right) e^{-\frac{t}{T}} = \frac{V}{RC} e^{-\frac{t}{RC}}$$

$$\text{rate of change of voltage}|_{t=6\text{ms}} = \frac{dV_C}{dt}|_{t=6\text{ms}} = 296.793 \text{ Volts/s}$$