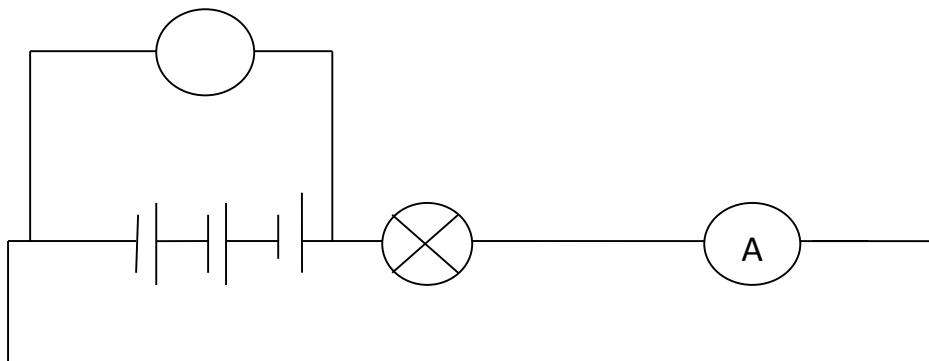


### Question #61551, Physics / Electric Circuits

Three 1.50V dry cells are connected in series to give a total voltage of 4.50V. A 12.0W lamp is connected in a circuit with the three dry cells.

a) Draw a schematic circuit diagram showing the dry cells and the lamp. Place an ammeter in the circuit to measure the current through the circuit. Place a voltmeter in the circuit to measure the potential different across the battery.



#### The answer to the question.

Indications voltmeter: 4.50 V

Indications ammeter:  $I = \frac{P}{V} = \frac{12\text{ W}}{4.5\text{ V}} = 2.67\text{ A}$