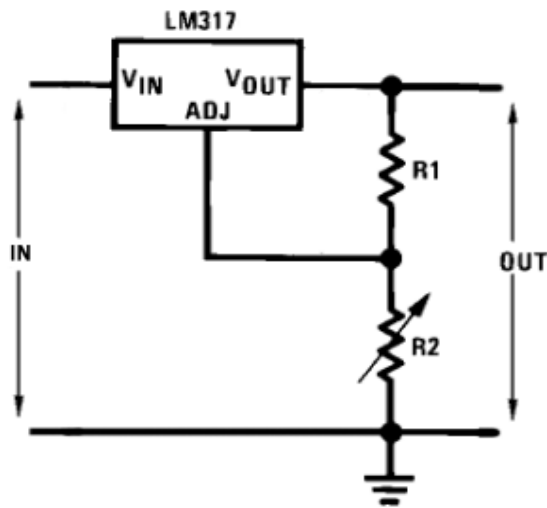


Answer on Question #65927 – Physics / Electric Circuits | Complete

Design and draw the circuit of a regulated power supply using LM 317 to provide 30V output.

Solution.

Classic circuit design of a regulated power supply for LM 317:



1. Calculating the ratio of the resistors values:

$$V_{out} = V_{ref} \left(1 + \frac{R_2}{R_1} \right) + I_{adj};$$

$$30 = 1,25 \left(1 + \frac{R_2}{R_1} \right);$$

$$\frac{R_2}{R_1} = 23;$$

2. We can take any resistor R1 value from 100 Ohm to 1000 Ohm, and calculate the resistor R2

$$R_1 = 100 \text{ Ohm};$$

$$R_2 = 100 * 23 = 23000 \text{ Ohm} = 23 \text{ kOhm};$$

Answer

$$R_1 = 100 \text{ Ohm};$$

$$R_2 = 23 \text{ kOhm};$$