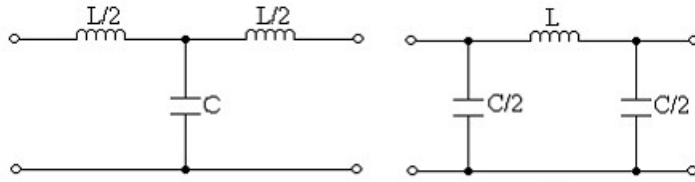


Answer on Question #75502, Physics Electric Circuits

Prove that the LC band pass filter is a constant K type filter.

Solution.



Resistance longitudinal and transverse branch:

$$Z_1 = j \cdot \omega \cdot L$$

$$Z_2 = \frac{1}{j \cdot \omega \cdot C}$$

Find the product of these resistances:

$$Z_1 \cdot Z_2 = \frac{j \cdot \omega \cdot L}{j \cdot \omega \cdot C} = \frac{L}{C} = k$$

We see that the product of the resistance of the filter branches, consisting of reactive elements, does not depend on the frequency and is equal to a constant number k . Such filters are called k -filters.

Answer provided by <https://www.AssignmentExpert.com>