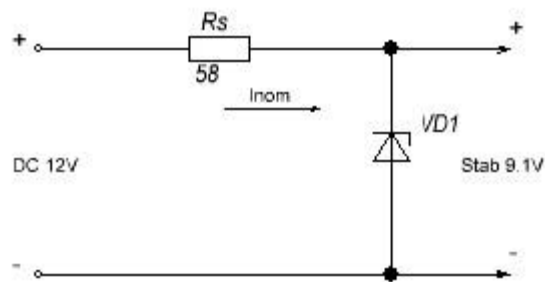


## Answer on Question #75508 - Physics / Electric Circuits

Design a zener regulated power supply to give 9.1V DC output with maximum load current of 50 mA. Assume that the minimum  $I_z$  required for proper functioning of zener diode is 5 mA, and the unregulated DC input is 12V. Indicate the value of  $R_s$  and power ratings of zener diode and  $R_s$ .

**Solution.**



$$I = \frac{U}{R}; R = \frac{U}{I}; U_{R_s} = 12V - 9.1V = 2.9V; R_s = \frac{U_{R_s}}{I} = \frac{2.9V}{0.05A} = 58 \text{ Ohm}$$

$$P_{R_s} = I^2 * R_{R_s} = 0.05^2 * 58 = 0.145W$$

$$P_{V_{d1}} = U * I = 9.1V * 0.05A = 0.455W$$

**Answer.**  $R_s=58 \text{ Ohm}$ ,  $P_{R_s}=0.145W$ ,  $P_{V_{d1}}=0.455W$