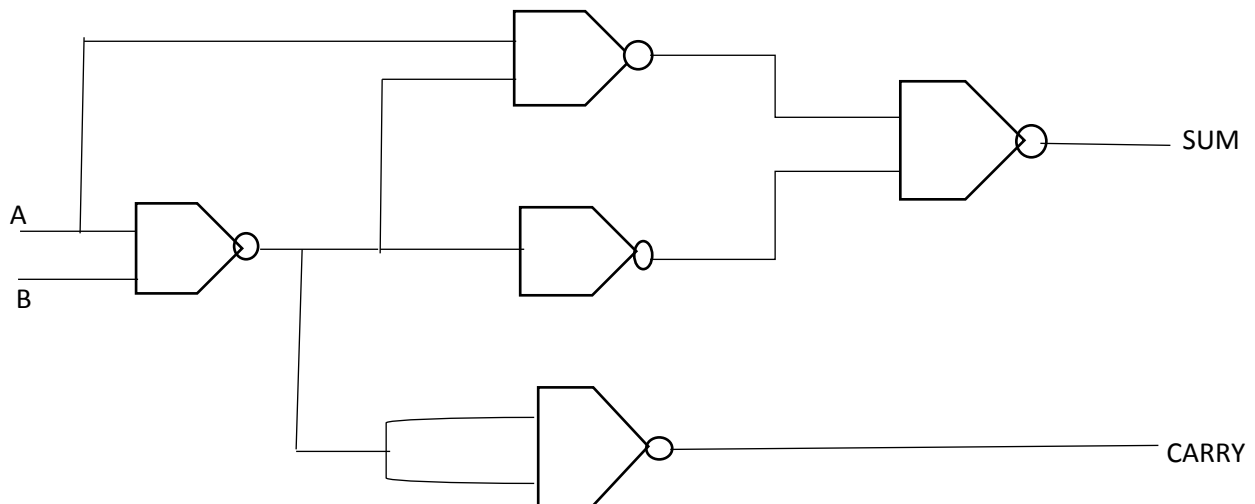



Answer on Question # 76629, Physics -Electric Circuits:

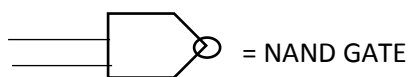Question: Draw a half adder circuit using only NAND gates.

Solution:



CIRCUIT DIAGRAM OF HALF-ADDER USING NAND GATES



A and B are the two inputs in the circuit diagram and outputs are sum and carry.

Answer: Circuit diagram shows half adder circuit using two input NAND gates.

Answer provided by <https://www.AssignmentExpert.com>