

Answer on Question #79555, Physics / Other

The intensity of a lightbulb with a resistance of 110 ohms is controlled by connecting it in series with an inductor whose inductance can be varied from $L=0$ to $L=L_{max}$. This "light dimmer" circuit is connected to an ac generator with frequency of 60 Hz and an rms voltage of 120V. $P=130$ w The inductor is now adjusted to $L=L_{max}$. The average power dissipated in the lightbulb is one-fourth of 130 W. What is the value of L_{max} ?

Solution:

The rms current flowing in the circuit:

$$I = \frac{V}{Z}$$

where, Z is impedance of the circuit.

$$Z = \sqrt{R^2 + \omega^2 L_{max}^2}$$

The average power dissipated of the circuit is

$$P_{av} = VI \cos \phi$$

The power factor of the circuit

$$\cos \phi = \frac{R}{Z}$$

$$P_{av} = \frac{V^2 R}{Z^2} = \frac{1}{4} \times 130 \text{ W}$$

$$\frac{V^2 R}{R^2 + \omega^2 L_{max}^2} = 32.5 \text{ W}$$

So,

$$L_{max} = \frac{1}{\omega^2} \left(\frac{V^2 R}{32.5} - R^2 \right) = \frac{1}{4\pi^2 f^2} \left(\frac{V^2 R}{32.5} - R^2 \right)$$

$$L_{max} = \frac{1}{4\pi^2 (60)^2} \left(\frac{120^2 \times 110}{32.5} - 110^2 \right) = 0.258 \text{ H}$$

Answer: 0.258 H

Answer provided by <https://www.AssignmentExpert.com>