


## ANSWER on Question #82274 – Physics – Electric Circuits

### QUESTION

Calculate the total resistance in the circuit below and the value of  $R_1 = 4\Omega$ ,  $R_2 = 1\Omega$ ,  $R_3 = 12\Omega$ ,  $R_4 = 8\Omega$
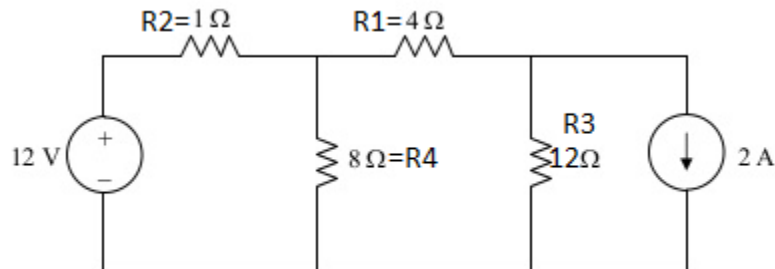
### SOLUTION

*Hint:* Since the electrical circuit is not given in the task, then how are the resistors with the given resistances arranged, then I will solve this problem using the drawing I found on the Internet.



Resistors  $R_1$  and  $R_3$  are connected in series, so they can be replaced with a single resistor with a resistance

$$R_{1-3} = R_1 + R_3 = 4\Omega + 12\Omega = 16\Omega$$

Resistors  $R_{1-3}$  and  $R_4$  are connected in parallel, so they can be replaced with a single resistor with a resistance

$$\frac{1}{R_{1-3-4}} = \frac{1}{R_{1-3}} + \frac{1}{R_4} \rightarrow \frac{1}{R_{1-3-4}} = \frac{1}{16} + \frac{1}{8} = \frac{1}{16} + \frac{2}{16} = \frac{3}{16} \rightarrow \frac{1}{R_{1-3-4}} = \frac{3}{16}$$

$$R_{1-3-4} = \frac{16}{3}\Omega$$

Resistors  $R_{1-3-4}$  and  $R_2$  are connected in series, so they can be replaced with a single resistor with a resistance

$$R_{1-2-3-4} = 1\Omega + \frac{16}{3}\Omega = \frac{3 + 16}{3}\Omega \rightarrow R_{1-2-3-4} = \frac{19}{3}\Omega \approx 6.33\Omega$$

### ANSWER

$$R_{1-2-3-4} = \frac{19}{3}\Omega \approx 6.33\Omega$$

Answer provided by <https://www.AssignmentExpert.com>